

# A study on the Moog 904b high pass filter

Diego Di Carlo, Mattia Paterna

Aalborg Universitet København

June 14, 2016

# Outcome

- 1 Introduction
- 2 Analysis of the analog filter
- 3 Discretization and Implementation

# Goal of the project

- Analyse the original analog circuit
- Get tuned-frequency behaviour given control voltage  $E$
- Replicate the circuit in discrete-time

# General overview

What is a Moog 904b?

- A voltage controlled filter, or **VCF**
- Built on Moog's late-60s filter patent
- Exhibits a high pass behaviour



# General overview

## Inside the module

- 4-pole high pass filter configuration
- 24 dB/oct (80dB/dec) attenuation for frequencies below  $\omega_c$
- frequency range switch to tune the whole frequency band

# Specifics

## US patent

- adder stage
- inverter stage
- four identical stages of PNP-NPN coupled transistors, working as voltage control resistor

# Specifics

The audio part

- $\sim 40$  dB attenuation stage
- 4 RC-circuit filtering stage
- output amplifier (+42 dB)

# Specifics

## Sziklay pair

- unity-gain op-amp
- make each stage independent

## Frequency range switch

- decoupling capacitors
- $1 + \frac{1}{2}$  octaves shifting



# Circuit Analysis

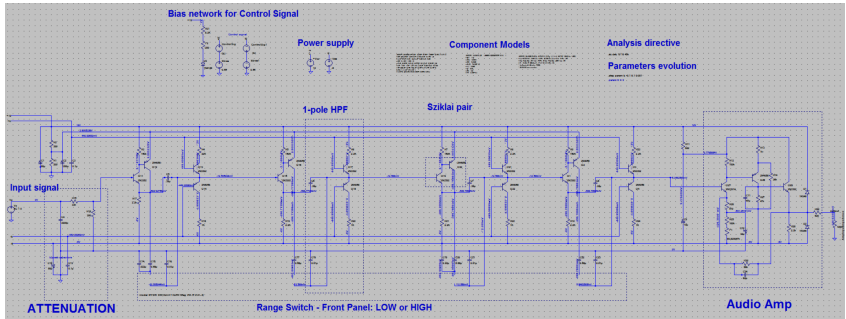


Figure: SPICE model version of only the audio part of the circuit subtitled with "DATE 6/23/70 DWG. NO 1118".

# DC Analysis


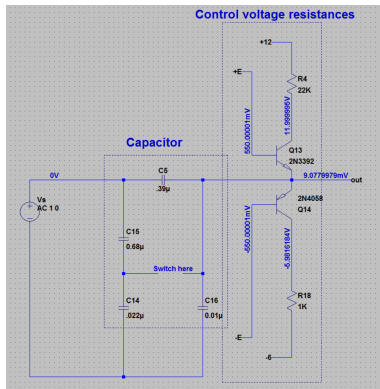


Figure: SPICE model version of only one high pass module

# AC Analysis

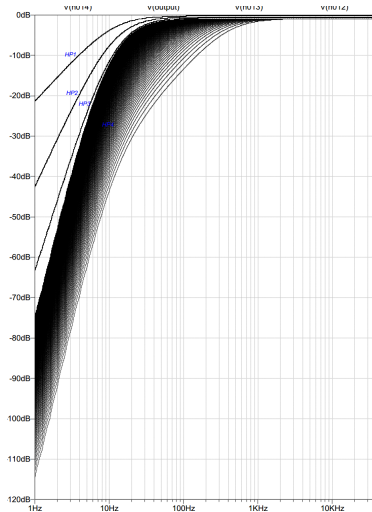

# AC Analysis

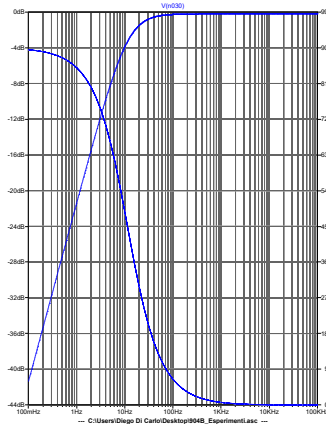


Figure: The transfer function (magnitude and phase) of a one *single-pole HPF stage*

# Laplace Analysis

Generalized *Ohm's Law*:

$$V(s) = \dot{Z}(s)I(s) \quad (1)$$

The quantity  $\dot{Z}(s) = \frac{V(s)}{I(s)}$  is called *impedance* of the circuit element.  
It assumes values in  $\mathbb{C}$  and in *Cartisian form* is defined as

$$\dot{Z}(s) = R(s) + jX(s) \quad (2)$$

where  $R(s)$  is called *resistance* and  $X(s)$  *reactance*.

# Laplace Analysis

## Impedance of Resistor and Capacitor

The **resistor** is a linear time-invariant and frequency-constant component:

$$\dot{Z}_R(s) = R, \forall s \in \mathbb{C}, \forall t \in \mathbb{R}. \quad (3)$$

The **capacitors** is a non-linear component:

$$i(t) = C \frac{dv(t)}{dt} \Leftrightarrow v(t) = \frac{1}{C} \int_0^\infty i(t) dt \quad (4)$$

where  $C$  is the capacitance of the capacitor.


If we apply the Laplace transform,

$$V(s) = \frac{1}{C} \frac{1}{s} I(s) \Rightarrow \dot{Z}_C(s) = \frac{1}{sC} \quad (5)$$

We find the impedance of the capacitor.

# Laplace Analysis

## Complex Signal Voltage Divider

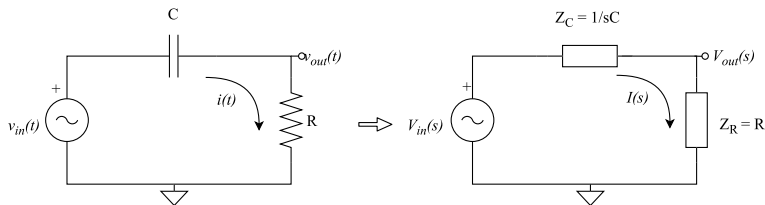

**Figure:** RC circuit as a voltage divider with complex impedances in Laplace domain

# Laplace Analysis

The RC circuit can be seen as a voltage divider of complex impedences for complex signals:

$$V_{\text{out}}(s) = \frac{\dot{Z}_R}{\dot{Z}_R + \dot{Z}_C} V_{\text{in}}(s) = \frac{R}{R + \frac{1}{sC}} V_{\text{in}}(s) \quad (6)$$

Rearranging the equation we obtain:

$$V_{\text{out}}(s) = \frac{s}{s + \frac{1}{RC}} V_{\text{in}}(s) \quad (7)$$

which is the well-know relation for an first order high pass filter (HPF) with cut-off frequency  $\omega_c = 1/RC$



# Laplace Analysis

Total transfer functions

The  $i$ -th stage single-pole HPF transfer function:


$$H_i(s) = \frac{V_{i,\text{out}}(s)}{V_{i,\text{in}}(s)} = \frac{s}{s + \omega_c} \quad (8)$$

Thus, overall transfer function  $H_{\text{HPF}}(s)$  considering all the 4 stages is:

$$\begin{aligned} H_{\text{HPF}}(s) &= H_1(s)H_2(s)H_3(s)H_4(s) \\ &= \frac{s^4}{s^4 + 4\omega_c s^3 + 6\omega_c^2 s^2 + 4\omega_c^3 s + \omega_c^4} \end{aligned} \quad (9)$$

## R and C derivation


Transistor as variable resistor

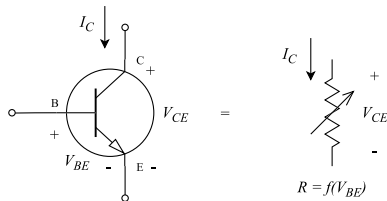

**Figure:** BJT NPN transistor as voltage-controlled resistor. The equivalent resistance  $R$  is a non-linear function of the voltage  $V_{BE}$

## R and C derivation

BJT's Voltage-current characteristic

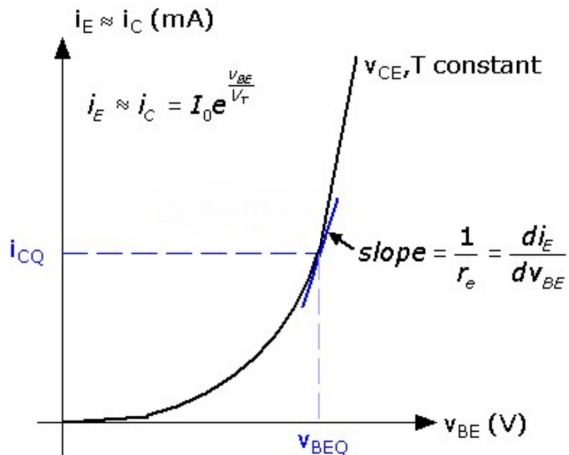

# R and C derivation

Resistance definition:

$$R = \frac{V}{I} \Rightarrow \frac{1}{R} = \frac{I}{V} \quad (10)$$

But for non linear voltage-current characteristics:

$$\frac{1}{R} = \frac{di(t)}{dv(t)} \quad (11)$$

The collector current value:

$$i_C = I_S \cdot e^{\frac{v_{BE}}{V_T}} \left( 1 + \frac{v_{CB}}{V_A} \right) \quad (12)$$

which usually is simplified as

$$i_C = I_S \cdot e^{\frac{v_{BE}}{V_T}} \left( 1 + \frac{v_{CE}}{V_A} \right) \quad (13)$$



# R and C derivation

## Dynamic (emitter) resistance evaluation

In our case, we have that  $v_{BE} = +E$ . To evaluate the dynamic equivalent resistance of this component, we must compute the derivative now.

$$\frac{1}{R} = \frac{\partial i_C}{\partial v_{CE}} = \frac{I_S \cdot e^{\frac{v_{+E}}{V_T}}}{V_A} \quad (14)$$

# R and C derivation

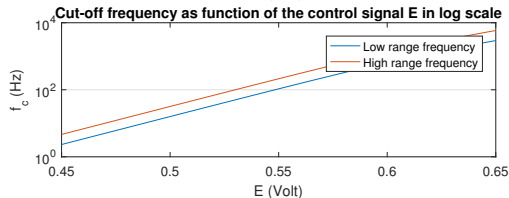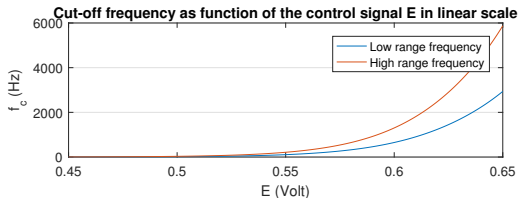


# Discretization

## Criteria

- topology preservation
- good transfer function replacement
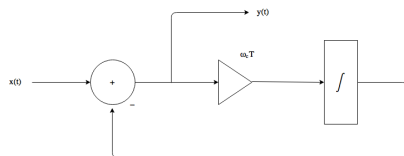
# Integrators

- $\omega_c$  express  $1/RC$
- the output signal is the resistor voltage
- the integrator is a gain element with factor  $\frac{1}{s}$






# Integrators

- several models for digital integrators
- different models yield to different transfer function
- the integrator is replaced by a unit-delay
- trapezoidal integration
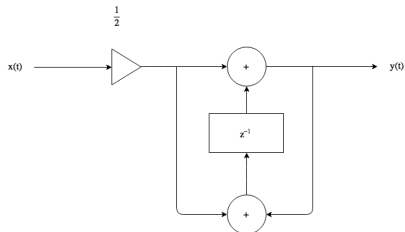
# Trapezoidal integrator

- precise mapping of analog frequency response
- preserve the original structure
- named **topology-preserved** transform



# Trapezoidal integrator

Its **transfer function** is

$$H(s) = \frac{\omega_c}{s} \Rightarrow H(z) = \frac{\omega_c}{2} \frac{1 + z^{-1}}{1 - z^{-1}}$$

that is the **bilinear** transform.

# Implementation

The proposed implementation consists of

- four identical trapezoidal integrators
- frequency provided in terms of **voltage tension**
- control for frequency range switch
- gentle saturation before the filtering stage

# Implementation


We've closely followed these models:

- Zavalishin's implementation of trapezoidal integrator
- Pirkle's general structure of Ladder Filter
- Välimäki and Huovilainen's saturation stage

# Evaluation

- square wave used
- the 904b could be considered as a ladder filter without recursion
- for  $E = 0.05$  we get 1954.2 Hz for the *High* setting and a frequency value of 651.39 Hz for the *Low* one, that is exactly a  $1 + \frac{1}{2}$  octaves shifting

# Evaluation

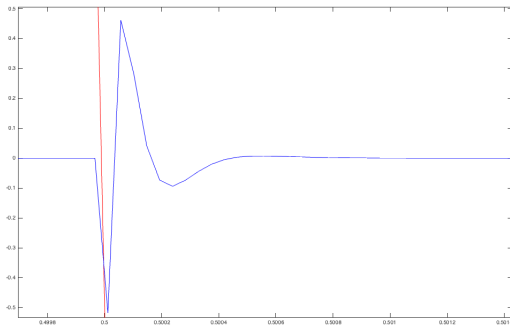

**Figure:** Effect of the discretized 904B on a pulse wave with duty cycle of 0.5. It can be noticed how the filter has a *smoothly* action on the square wave.

That's all, folks!